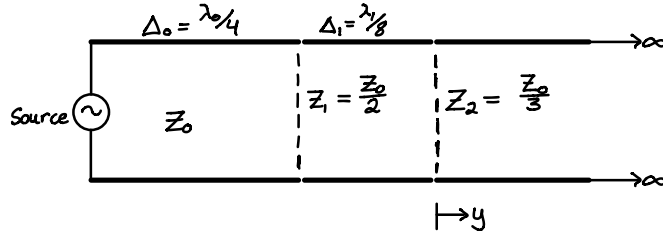


10.3 Impedance Transformation III

Given the following Transmission line:



10.1.3 Hand Calculation

Impedance Continuity states:

$$Z_1(0) = Z_2(0)$$

Since Z_2 line continues to ∞ , $\tilde{\Gamma}_2(y) = 0$ due to no reflected wave, then:

$$Z_1 \left(\frac{1 + \tilde{\Gamma}_1(0)}{1 - \tilde{\Gamma}_1(0)} \right) = Z_2$$

then $\tilde{\Gamma}_1(0)$ can be found as:

$$\tilde{\Gamma}_1(0) = \left(\frac{Z_2/Z_1 - 1}{Z_2/Z_1 + 1} \right) \quad * \quad \frac{Z_2}{Z_1} = \frac{Z_0/3}{Z_0/2} = \frac{2}{3}$$

$$\tilde{\Gamma}_1(0) = \left(\frac{\frac{2}{3} - 1}{\frac{2}{3} + 1} \right) = -\frac{1}{5}$$

Then:

$$\tilde{\Gamma}_1(-\lambda/8) = \tilde{\Gamma}_1(0) e^{j 2 \frac{2\pi}{\lambda} \frac{\lambda}{8}}$$

$$= \tilde{\Gamma}_1(0) e^{j \pi/4}$$

$$= +j \frac{1}{5}$$

From this the impedance $Z_1(-\lambda/8)$ can be found:

$$Z_1(-\lambda/8) = Z_1 \left(\frac{1 + \tilde{\Gamma}_1(-\lambda/8)}{1 - \tilde{\Gamma}_1(-\lambda/8)} \right)$$

$$= Z_1 \left(\frac{1 + j \frac{1}{5}}{1 - j \frac{1}{5}} \right)$$

Using MatLAB:

$$Z_1(-\lambda/8) = Z_1 \left(\frac{1}{3} - j \frac{5}{13} \right) = Z_1 (1 e^{-j 0.1257 \pi}) = \frac{1}{2} Z_0 \angle +22.62 \quad * \quad \tan^{-1} \left(\frac{5}{13} \right) \approx 0.1257 \pi$$

then from 2nd Boundary at $-\lambda/8$:

Impedance Continuity

$$Z_0(-\lambda/8) = Z_1(-\lambda/8)$$

$$Z_0 \left(\frac{1 + \tilde{S}_0(-\lambda/8)}{1 - \tilde{S}_0(-\lambda/8)} \right) = Z_1 e^{-j0.1257\pi} \quad * \quad Z_1 = \frac{Z_0}{2}$$

$$\frac{1 + \tilde{S}_0(-\lambda/8)}{1 - \tilde{S}_0(-\lambda/8)} = \frac{1}{2} e^{-j0.1257\pi}$$

$$S_0(-\lambda/8) = \left(\frac{\frac{1}{2} e^{j0.1257\pi} - 1}{\frac{1}{2} e^{j0.1257\pi} + 1} \right) \quad * \quad Z_1 = Z_0/2$$

$$\tilde{S}_0(-\lambda/8) = \left(\frac{\frac{1}{2} e^{j0.1257\pi} - 1}{\frac{1}{2} e^{j0.1257\pi} + 1} \right)$$

Computing w/ MATLAB

$$\therefore \tilde{S}_0(-\lambda/8) \approx 0.388 \angle 152.85^\circ = 0.8492\pi$$

then:

$$S_0(-\Delta_1 - \Delta_0) \approx 0.388 e^{-j0.8492\pi} e^{j\frac{4\pi}{\lambda} \frac{\lambda}{4}} \quad * \text{ if } \lambda_0 = \lambda_1$$

$$\begin{aligned} \tilde{S}_0(-\Delta_1 - \Delta_0) &= 0.388 e^{-j0.8492\pi} e^{-j\pi} \\ &= 0.388 \angle -27.15^\circ = 0.388 e^{-j1.8492\pi} \end{aligned}$$

impedence at source can be found as:

$$\begin{aligned} Z_0(-\Delta_1 - \Delta_0) &= Z_0 \left(\frac{1 + \tilde{S}_0(-\Delta_1 - \Delta_0)}{1 - \tilde{S}_0(-\Delta_1 - \Delta_0)} \right) \\ &= Z_0 \left(\frac{1 - 0.388 e^{j1.85\pi}}{1 + 0.388 e^{j1.8\pi}} \right) \end{aligned}$$

Using MATLAB:

$$Z_0(-\Delta_1 - \Delta_0) = 2Z_0 \angle -22.62^\circ$$

Calculating using Smith chart

Normalized z :

$$\frac{Z_2}{Z_1} = \frac{1/3}{1/2} = 2/3 \Rightarrow r = 2/3, x = 0$$

Using Smith Chart :

Then the reflection is found as :

$$\tilde{\Gamma}_1(0) = -\frac{1}{5}$$

then $\tilde{\Gamma}_1(-\lambda/4) = \frac{1}{5}j$ * CW rotation of 90° due to $-\lambda/8$ position

From this impedance of Z_1 can be found at $-\lambda/8$

$$Z_1(-\lambda/8) = Z_1 \left(\frac{1 + \tilde{\Gamma}_1(-\lambda/8)}{1 - \tilde{\Gamma}_1(-\lambda/8)} \right)$$

$$\frac{Z_1(-\lambda/8)}{Z_1} = \left(\frac{1 + \frac{1}{5}j}{1 - \frac{1}{5}j} \right) = 0.9231 + 0.3846j$$

$$Z_1(-\lambda/8) = \frac{Z_0}{2} (0.9231 + 0.3846j)$$

$$Z_1(-\lambda/8) = Z_0 (0.4615 + 0.1923j)$$

so at $-\lambda/8$

$$\Gamma = 0.4615, \chi = -0.1923j$$

then S_0 can be found as :

$$\tilde{\Gamma}_0(-\lambda/8) = 0.3875 + 0.1875j$$

then moving to Source :

$$\tilde{\Gamma}_1(-\lambda/8 - \lambda/4) = 0.3875 - 0.1875j$$

then finally Z_0 at source can be found as :

$$Z_0(-\lambda/8 - \lambda/4) = \left(\frac{1 + (0.3875 - 0.1875j)}{1 - (0.3875 - 0.1875j)} \right)$$

$$\approx 2.186 \angle -24.72^\circ$$

The Complete Smith Chart

Black Magic Design

