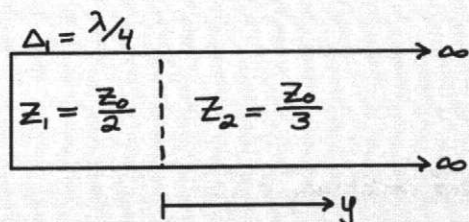


10.1 Impedance Transformation I

Given the Following Transmission line:

Compute $\tilde{\rho}_1(0)$ & $Z_1(-\lambda/4)$ by hand and using Smith Chart

10.1.1 Hand Calculation

Impedance Continuity states:

$$Z_1(0) = Z_2(0)$$

Where Spatially dependence says:

$$Z_n(y) = Z_n \left(\frac{1 + \tilde{\rho}_n(y)}{1 - \tilde{\rho}_n(y)} \right)$$

$$Z_1 \left(\frac{1 + \tilde{\rho}_1(0)}{1 - \tilde{\rho}_1(0)} \right) = Z_2 \left(\frac{1 + \tilde{\rho}_2(0)}{1 - \tilde{\rho}_2(0)} \right)$$

Since Z_2 impedance line goes to infinity, then no reflected wave is producedthus $\tilde{\rho}_2(y) = 0$ for all y

$$\therefore \frac{1 + \tilde{\rho}_1(0)}{1 - \tilde{\rho}_1(0)} = \frac{Z_2}{Z_1} \quad * Z_1 = \frac{Z_0}{2}, Z_2 = \frac{Z_0}{3}$$

$$\frac{1 + \tilde{\rho}_1}{1 - \tilde{\rho}_1} = \frac{2}{3} \quad * \tilde{\rho}_n(y) = \tilde{\rho}_n e^{2j\beta y} \rightarrow \tilde{\rho}_1(0) = \tilde{\rho} \text{ (some complex const)}$$

$$1 + \tilde{\rho}_1 = \frac{2}{3} - \frac{2}{3}\tilde{\rho}_1$$

$$\frac{5}{3}\tilde{\rho}_1 = -\frac{1}{3}$$

$$\boxed{\therefore \tilde{\rho}_1(0) = -\frac{1}{5}}$$

$$\tilde{\rho}_1(y) = -\frac{1}{5} e^{j\frac{4\pi}{\lambda}y}$$

$$* \beta = \frac{2\pi}{\lambda}$$

$$Z_1(-\lambda/4) = Z_1 \left(\frac{1 + \tilde{\rho}_1(-\lambda/4)}{1 - \tilde{\rho}_1(-\lambda/4)} \right)$$

$$* \tilde{\rho}_1 = -\frac{1}{5} e^{-j\pi} = \frac{1}{5} \quad ?$$

$$Z_1(-\lambda/4) = Z_1 \left(\frac{1 + j\frac{1}{3}}{1 - j\frac{1}{3}} \right) \quad \text{Signs wrong.}$$

$$= Z_1 \left(\frac{1 + \frac{1}{3}}{1 - \frac{1}{3}} \right)$$

$$\boxed{Z_1(-\lambda/4) = (3/2)Z_1} \quad \times$$

10.1.2 Smith Chart

1. Computing normalized impedance and associated normalized resistance r & x :

$$Z_1(0) = Z_2(0)$$

$$Z_1 \left(\frac{1 + \tilde{\Gamma}_1(0)}{1 - \tilde{\Gamma}_1(0)} \right) = Z_2 \left(\frac{1 + \tilde{\Gamma}_2(0)}{1 - \tilde{\Gamma}_2(0)} \right) \quad * \tilde{\Gamma}_2(0) = 0$$

$$\left(\frac{1 + \tilde{\Gamma}_1(0)}{1 - \tilde{\Gamma}_1(0)} \right) = \frac{Z_2}{Z_1}$$

$$\therefore \tilde{\Gamma}_1(0) = \left(\frac{Z_2/Z_1 - 1}{Z_2/Z_1 + 1} \right)$$

Normalized impedance is found as:

$$\frac{Z_2}{Z_1} = \frac{3}{2} = r + jx$$

$$\therefore r = 3/2, x = 0$$

2. from Smith Chart:

$$\tilde{\Gamma}_1(0) = -1/3$$

3. where:

$$\tilde{\Gamma}_1(-\lambda/4) = \tilde{\Gamma}_1(0) e^{j2\beta(-\lambda/4)} = \tilde{\Gamma}_1(0) \angle 2\beta(-\lambda/4) \quad * \phi = -2\beta\lambda/4 = -\pi$$

$$= 1/3 \text{ from Smith Chart using CW rotation of } -\pi \text{ from } \tilde{\Gamma}_1(0)$$

4. from the Smith Chart this yields:

$$\boxed{r = 3/2, x = 0} \quad \checkmark$$

5. Z_1 can be determined at $y = -\lambda$ as:

$$Z_1(-\lambda) = Z_1 \left(\frac{1 + \tilde{\Gamma}_1(-\lambda)}{1 - \tilde{\Gamma}_1(-\lambda)} \right) \quad * \tilde{\Gamma}_1(-\lambda) = 1/3$$


$$= Z_1 \left(\frac{1 + 1/3}{1 - 1/3} \right)$$

$$\boxed{Z_1(-\lambda) = \frac{3}{2} Z_1}$$

~ write in terms of Z_0 ! (which is given.)


The Complete Smith Chart

Black Magic Design

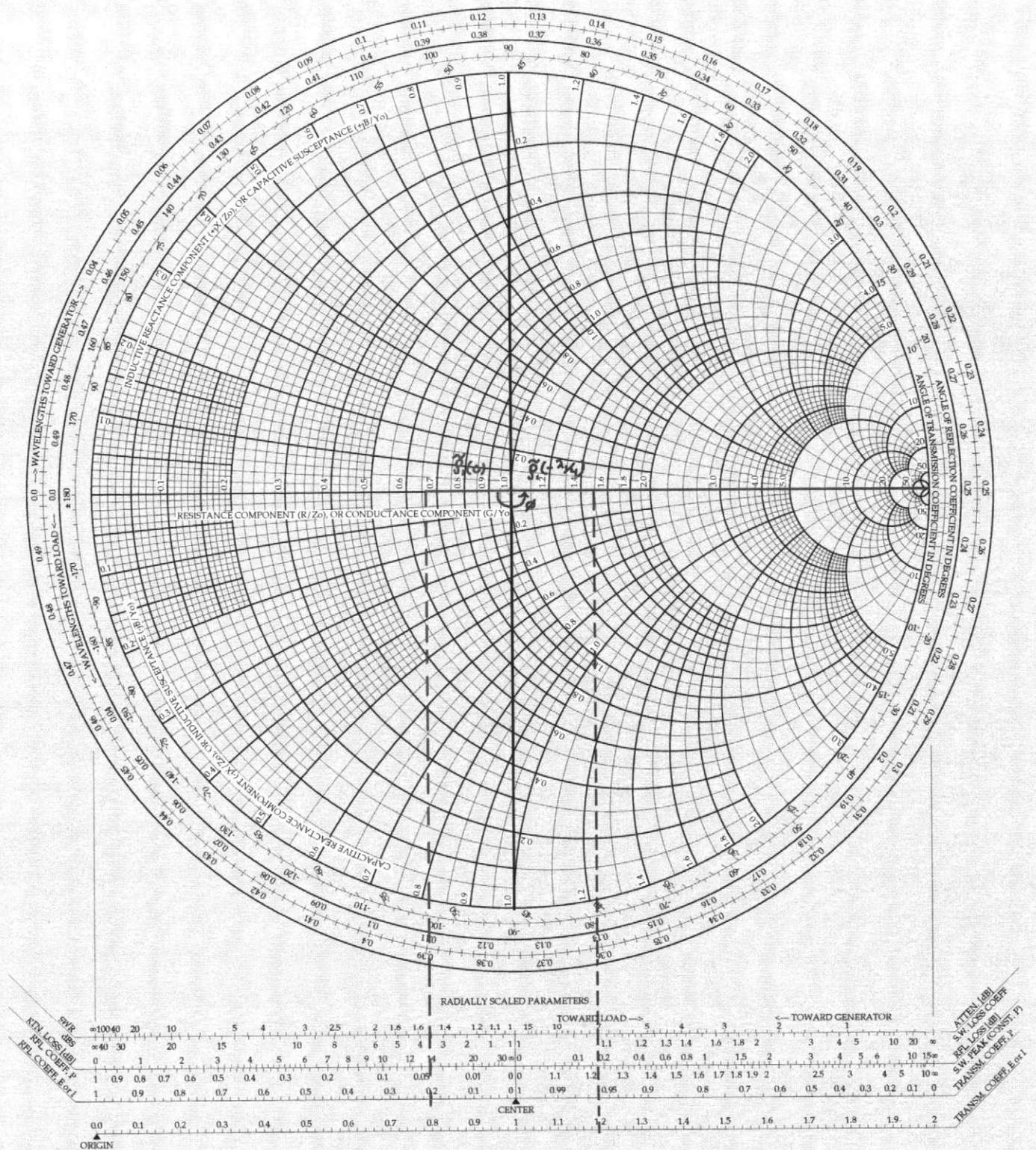

10.1 Impedance Transformation II

Given the Following Transmission line:

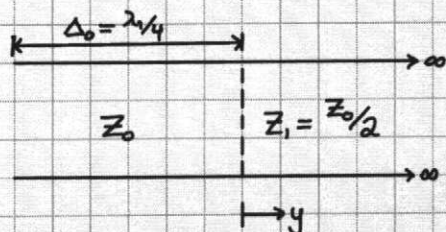

Compute:

1. $\tilde{\rho}_0(0)$
2. $Z_0(-\Delta_1)$

10.2.1 Hand Calculation

1. Impedance Continuity states:

$$Z_0(0) = Z_1(0)$$

Since Z_1 line exists and continues to ∞ , then no reflected wave exists:

$$\therefore \tilde{\rho}_1(y) = 0$$

$$Z_0 \left(\frac{1 + \tilde{\rho}_0(0)}{1 - \tilde{\rho}_0(0)} \right) = Z_1 \quad * Z_1 = Z_0/2$$

then $\tilde{\rho}_0(0)$ can be found as:

$$\begin{aligned} \tilde{\rho}_0(0) &= \left(\frac{Z_1/Z_0 - 1}{Z_1/Z_0 + 1} \right) \\ &= \left(\frac{\frac{1}{2} - 1}{\frac{1}{2} + 1} \right) \end{aligned}$$

$$\therefore \tilde{\rho}_0(0) = -1/3$$

2. To Find $Z_0(-\Delta_1)$, phase is added to $\tilde{\rho}_0(y)$:

$$\tilde{\rho}_0(-\Delta_0) = -1/3 e^{j2\beta_0(\Delta_1)} \quad * \beta_0 = \frac{2\pi}{\lambda_0} \text{ \& } \Delta_1 = \lambda/4$$

$$\tilde{\rho}_0(-\Delta_0) = -1/3 e^{-j\pi} \quad * \text{if } \lambda_1 = \lambda_0$$

$$= 1/3 \quad * e^{-j\pi} = -1$$

$$Z_0(-\Delta_0) = Z_0 \left(\frac{1 + \tilde{\rho}_0(-\Delta_0)}{1 - \tilde{\rho}_0(-\Delta_0)} \right)$$

$$= Z_0 \left(\frac{4/3}{2/3} \right) = 2Z_0$$

10.2.2 Using Smith Chart

1. Normalized impedance says:

$$\frac{Z_1(0)}{Z_0(0)} = \frac{1}{2}$$

then $r = \frac{1}{2}$, $x = 0$

2. From Smith Chart

$$\tilde{\rho}_0(0) = -\frac{1}{3}$$

3. Finding $\rho_0(-\lambda/4)$:

$$\tilde{\rho}_0(-\lambda/4) = \tilde{\rho}_0(0) e^{-j\frac{4\pi}{\lambda} \cdot \frac{\lambda}{4}}$$

$$= \tilde{\rho}_0(0) e^{-j\pi}$$

$$\tilde{\rho}_0(-\lambda/4) = -\tilde{\rho}_0(0) = \frac{1}{3}$$

4. From a CW rotation of π , the Smith Chart reads:

$$r \approx 2.0, \quad x = 0$$

5. Then


$$Z_0(-\lambda/4) = Z_0 \left(\frac{1 + \tilde{\rho}_0(-\lambda/4)}{1 - \tilde{\rho}_0(-\lambda/4)} \right)$$

$$= Z_0 \left(\frac{1 + \frac{1}{3}}{1 - \frac{1}{3}} \right)$$

$$= Z_0 \left(\frac{4}{3} \cdot \frac{3}{2} \right)$$


$$\boxed{Z_0(-\lambda/4) = 2Z_0}$$

Black Magic Design

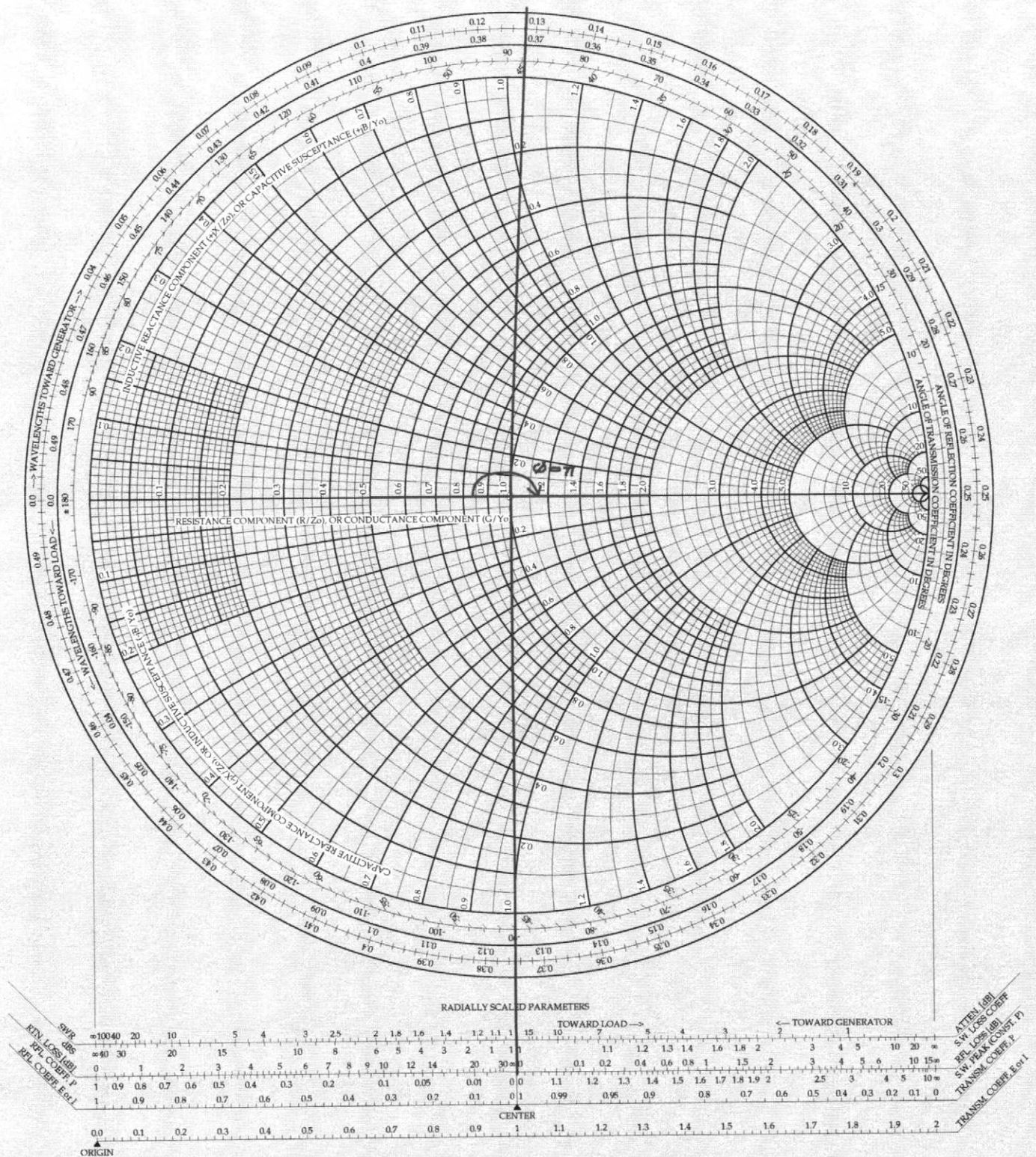

10.3 Impedance Transformation III

Given the following Transmission line:

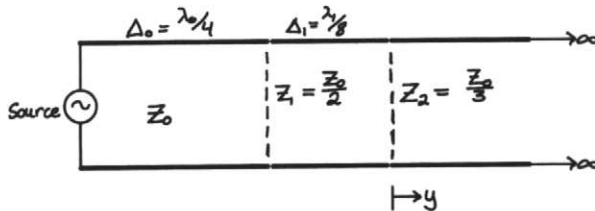

10.1.3 Hand Calculation

Impedance Continuity states:

$$Z_1(0) = Z_2(0)$$

Since Z_2 line continues to ∞ , $\tilde{\Gamma}_2(y) = 0$ due to no reflected wave, then:

$$Z_1 \left(\frac{1 + \tilde{\Gamma}_1(0)}{1 - \tilde{\Gamma}_1(0)} \right) = Z_2$$

then $\tilde{\Gamma}_1(0)$ can be found as:

$$\tilde{\Gamma}_1(0) = \left(\frac{Z_2/Z_1 - 1}{Z_2/Z_1 + 1} \right) \quad * \quad \frac{Z_2}{Z_1} = \frac{Z_0/3}{Z_0/2} = \frac{2}{3}$$

$$\tilde{\Gamma}_1(0) = \left(\frac{\frac{2}{3} - 1}{\frac{2}{3} + 1} \right) = -\frac{1}{5}$$

Then:

$$\begin{aligned} \tilde{\Gamma}_1(-\lambda/8) &= \tilde{\Gamma}_1(0) e^{j2\beta \cdot \lambda/8} \\ &= \tilde{\Gamma}_1(0) e^{-j\pi/4} \\ &= +j\frac{1}{5} \quad \checkmark \end{aligned}$$

From this the Impedance $Z_1(-\lambda/8)$ can be found:

$$\begin{aligned} Z_1(-\lambda/8) &= Z_1 \left(\frac{1 + \tilde{\Gamma}_1(-\lambda/8)}{1 - \tilde{\Gamma}_1(-\lambda/8)} \right) \\ &= Z_1 \left(\frac{1 + j\frac{1}{5}}{1 - j\frac{1}{5}} \right) \end{aligned}$$

Using MatLAB:

$$Z_1(-\lambda/8) = Z_1 \left(\frac{1 + j\frac{1}{5}}{1 - j\frac{1}{5}} \right) = Z_1 (1e^{-j0.1257\pi}) = \frac{1}{2} Z_0 * 22.62 \quad * \tan^{-1}\left(\frac{1}{5}\right) \approx 0.1257\pi$$

Why is this \oplus ?
given this \ominus

then from 2nd Boundary at $-\lambda/8$:

Impedance Continuity

$$Z_0(-\lambda/8) = Z_1(-\lambda/8)$$

$$Z_0 \left(\frac{1 + \tilde{S}_0(-\lambda/8)}{1 - \tilde{S}_0(-\lambda/8)} \right) = Z_1 e^{-j0.1257\pi} \quad * \quad Z_1 = \frac{Z_0}{2}$$

$$\frac{1 + \tilde{S}_0(-\lambda/8)}{1 - \tilde{S}_0(-\lambda/8)} = \frac{1}{2} e^{-j0.1257\pi}$$

$$\tilde{S}_0(-\lambda/8) = \left(\frac{\frac{1}{2} e^{j0.1257\pi} - 1}{\frac{1}{2} e^{j0.1257\pi} + 1} \right) * Z_1 = Z_0/2$$

$$\tilde{S}_0(-\lambda/8) = \left(\frac{\frac{1}{2} e^{j0.1257\pi} - 1}{\frac{1}{2} e^{j0.1257\pi} + 1} \right)$$

Computing w/ MATLAB

$$\therefore \tilde{S}_0(-\lambda/8) \approx 0.388 \angle 152.85^\circ = 0.8492\pi$$

then:

$$\tilde{S}_0(-\Delta_1 - \Delta_0) \approx 0.388 e^{-j0.8492\pi} e^{j\frac{4\pi}{25} \frac{24}{\pi}} \quad * \text{ if } \lambda_0 = \lambda_1$$

$$\tilde{S}_0(-\Delta_1 - \Delta_0) = 0.388 e^{-j0.8492\pi} e^{-j\pi}$$

$$= 0.388 \angle -27.15^\circ = 0.388 e^{-j1.8492\pi}$$

impedance at source can be found as:

$$\begin{aligned} Z_0(-\Delta_1 - \Delta_0) &= Z_0 \left(\frac{1 + \tilde{S}_0(-\Delta_1 - \Delta_0)}{1 - \tilde{S}_0(-\Delta_1 - \Delta_0)} \right) \\ &= Z_0 \left(\frac{1 - 0.388 e^{j1.85\pi}}{1 + 0.388 e^{j1.85\pi}} \right) \end{aligned}$$

Using MATLAB:

$$Z_0(-\Delta_1 - \Delta_0) = 2Z_0 \angle -22.62^\circ$$

Calculating using Smith chart

Normalized z :

$$\frac{Z_2}{Z_1} = \frac{1/3}{1/2} = 2/3 \Rightarrow r = 2/3, x = 0$$

Using Smith Chart :

Then the reflection is found as :

$$\tilde{\Gamma}_1(0) = -\frac{1}{5}$$

then $\tilde{\Gamma}_1(-\lambda_4) = \frac{1}{5}j$ * CW rotation of 90° due to $-\lambda_8$ position

From this impedance of Z_1 can be found at $-\lambda_8$

$$Z_1(-\lambda_8) = Z_1 \left(\frac{1 + \tilde{\Gamma}_1(-\lambda_8)}{1 - \tilde{\Gamma}_1(-\lambda_8)} \right)$$

$$\frac{Z_1(-\lambda_8)}{Z_1} = \left(\frac{1 + \frac{1}{5}j}{1 - \frac{1}{5}j} \right) = 0.9231 + 0.3846j$$

$$Z_1(-\lambda_8) = \frac{Z_0}{2} (0.9231 + 0.3846j)$$

$$Z_1(-\lambda_8) = Z_0 (0.4615 + 0.1923j)$$

so at $-\lambda_8$

$$\Gamma = 0.4615, \chi = -0.1923j$$

then S_0 can be found as :

$$\tilde{\Gamma}_0(-\lambda_8) = 0.3875 + 0.1875j$$

then moving to Source :

$$\tilde{\Gamma}_1(-\lambda_8 - \lambda_4) = 0.3875 - 0.1875j$$

then finally Z_0 at source can be found as :

$$Z_0(-\lambda_8 - \lambda_4) = \left(\frac{1 + (0.3875 - 0.1875j)}{1 - (0.3875 - 0.1875j)} \right)$$

$$\approx 2.186 \angle -24.72^\circ$$

The Complete Smith Chart

Black Magic Design

