
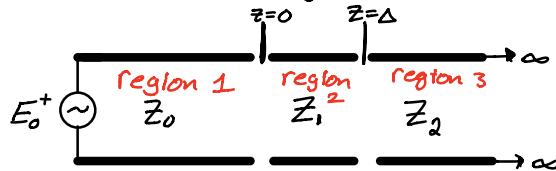


9.2.1

Given the following Transmission line:

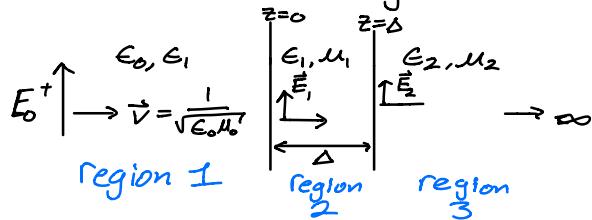

where the equivalent region can be described as an electric field entering different dielectric regions



Let each region be denoted by n ($n=0, 1, 2$)

Electric potential at each region can be described as a forward & backward travelling voltage :

$$\tilde{V}_n(z) = \tilde{V}_n^+ e^{-j\beta_n z} + \tilde{V}_n^- e^{j\beta_n z}$$

Similarly, the electric field in each can be written in the form of a forward/backward travelling electric field.

$$\tilde{E}_n(z) = \tilde{E}_n^+ e^{-jk_n z} + \tilde{E}_n^- e^{jk_n z}$$

Where the corresponding Real Potential & Electric fields can be given as:

$$E_n(z, t) = \operatorname{Re} [\tilde{E}_n(z) e^{j\omega t}]$$

$$V_n(z, t) = \operatorname{Re} [\tilde{V}_n(z) e^{j\omega t}]$$

If given a V_0^+ . At $z=0$ and $z=\Delta$, potential & current must be continuous (equivalently E & H must be continuous from Maxwell's B.C.'s). Also assume region 2 extends to infinity such that $V_2^- = 0$

Considering Steady State :

when looking at $z=0$:

Voltage Continuity states:

$$\tilde{V}_o(0) = \tilde{V}_i(0)$$

$$\textcircled{1} \quad \tilde{V}_o^+ + \tilde{V}_o^- = \tilde{V}_i^+ + \tilde{V}_i^-$$

Similarly for Current Continuity equation

$$\tilde{I}_o(0) = \tilde{I}_i(0)$$

at $z=0$

$$\textcircled{2} \quad \tilde{V}_o^+ - \tilde{V}_o^- = \frac{Z_0}{Z_1} (\tilde{V}_i^+ - \tilde{V}_i^-)$$

Similarly doing this for Boundary 2:

$$\tilde{V}_i(\Delta) = \tilde{V}_2(\Delta)$$

$$\tilde{V}_1^+ e^{-j\beta_1 \Delta} + \tilde{V}_1^- e^{j\beta_1 \Delta} = \tilde{V}_2^+ e^{j\beta_2 \Delta} + \tilde{V}_2^- e^{j\beta_2 \Delta}$$

* recall $\tilde{V}_2^- = 0$, no reflection, then:

$$\textcircled{3} \quad \tilde{V}_1^+ e^{-j\beta_1 \Delta} + \tilde{V}_1^- e^{j\beta_1 \Delta} = \tilde{V}_2^+ e^{-j\beta_2 \Delta}$$

Applying this to current continuity:

$$\tilde{I}_1(\Delta) = \tilde{I}_2(\Delta)$$

$$\textcircled{4} \quad \tilde{V}_1^+ e^{-j\beta_1 \Delta} - \tilde{V}_1^- e^{j\beta_1 \Delta} = \frac{Z_1}{Z_2} (\tilde{V}_2^+ e^{-j\beta_2 \Delta})$$

adding eqns $\textcircled{3} \& \textcircled{4}$:

$$2\tilde{V}_1^+ e^{-j\beta_1 \Delta} = \tilde{V}_2^+ (1 + \frac{Z_1}{Z_2}) e^{-j\beta_2 \Delta}$$

$$\tilde{V}_2^+ = \left(\frac{2}{1 + \frac{Z_1}{Z_2}} \right) \tilde{V}_1^+ e^{-j(\beta_1 - \beta_2)\Delta} \quad * \text{Let } \tau_2 = \frac{2}{1 + \frac{Z_1}{Z_2}}$$

$$\therefore \tilde{V}_2^+ = \tau_2 \tilde{V}_1^+ e^{-j(\beta_1 - \beta_2)\Delta}$$

Subtracting: $\textcircled{4} - \left(\frac{Z_1}{Z_2} \right) \textcircled{3}$

$$\tilde{V}_1^+ e^{-j\beta_1 \Delta} - \tilde{V}_1^- e^{j\beta_1 \Delta} - \frac{Z_1}{Z_2} (\tilde{V}_1^+ e^{-j\beta_1 \Delta} + \tilde{V}_1^- e^{j\beta_1 \Delta}) = 0$$

$$\tilde{V}_1^+ (1 - \frac{Z_1}{Z_2}) e^{-j\beta_1 \Delta} = \tilde{V}_1^- (1 + \frac{Z_1}{Z_2}) e^{j\beta_1 \Delta}$$

$$\tilde{V}_1^- = \left(\frac{1 - \frac{Z_1}{Z_2}}{1 + \frac{Z_1}{Z_2}} \right) e^{-j2\beta_1 \Delta} \tilde{V}_1^+ \quad * \text{Let } \rho_2 = \frac{Z_2 - Z_1}{Z_2 + Z_1}$$

$$\text{Then: } \tilde{V}_1^- = S_2 e^{-j2B\Delta} \tilde{V}_1^+$$

Can now rewrite eqn ① & ②:

$$① \quad \tilde{V}_o^+ + \tilde{V}_o^- = \tilde{V}_1^+ (1 + S_2 e^{-j2B\Delta})$$

$$② \quad \tilde{V}_o^+ - \tilde{V}_o^- = \frac{Z_o}{Z_1} \tilde{V}_1^+ (1 - S_2 e^{-j2B\Delta})$$

Adding: ① + ②

$$2 \tilde{V}_o^+ = [(1 + S_2 e^{-j2B\Delta}) + \frac{Z_o}{Z_1} (1 - S_2 e^{-j2B\Delta})] \tilde{V}_1^+$$

$$\frac{2 \tilde{V}_o^+}{(1 + S_2 e^{-j2B\Delta}) + \frac{Z_o}{Z_1} (1 - S_2 e^{-j2B\Delta})} = \tilde{V}_1^+$$

* Let $\alpha = S_2 e^{-j2B\Delta}$

$$\tilde{V}_1^+ = \frac{2 \tilde{V}_o^+}{(1 + \frac{Z_o}{Z_1}) + \alpha (1 - \frac{Z_o}{Z_1})}$$

then: $\tilde{V}_1^+ = \frac{2 \tilde{V}_o^+}{(1 + \alpha) + \frac{Z_o}{Z_1} (1 - \alpha)} \quad * \quad \gamma_1 = \frac{2}{(1 + \alpha) + \frac{Z_o}{Z_1} (1 - \alpha)}$

$$\tilde{V}_1^+ = \gamma_1 \tilde{V}_o^+$$

Similarly: ② - $\frac{Z_o}{Z_1} ①$

$$\tilde{V}_o^+ - \tilde{V}_o^- - \frac{Z_o}{Z_1} (\tilde{V}_o^+ + \tilde{V}_o^-) = \frac{Z_o}{Z_1} \tilde{V}_1^+ (1 - \alpha) - \frac{Z_o}{Z_1} \tilde{V}_1^+ (1 + \alpha)$$

$$(1 - \frac{Z_o}{Z_1}) \tilde{V}_o^+ - (1 + \frac{Z_o}{Z_1}) \tilde{V}_o^- = -2 \frac{Z_o}{Z_1} \alpha \tilde{V}_1^+$$

* $\tilde{V}_1^+ = \gamma_1 \tilde{V}_o^+$

$$[(1 - \frac{Z_o}{Z_1}) + 2 \frac{Z_o}{Z_1} \alpha] \tilde{V}_o^+ = (1 + \frac{Z_o}{Z_1}) \tilde{V}_o^-$$

$$\tilde{V}_o^- = \underbrace{\left(\frac{1 - \frac{Z_o}{Z_1}}{1 + \frac{Z_o}{Z_1}} \right)}_{S_1} \tilde{V}_o^+ + \underbrace{\left(\frac{2}{1 + \frac{Z_o}{Z_1}} \right)}_{\gamma_0} \frac{Z_o}{Z_1} \alpha \tilde{V}_o^+$$

$$\tilde{V}_o^- = S_1 \tilde{V}_o^+ + \gamma_0 \alpha \tilde{V}_o^+$$

$$\boxed{\tilde{V}_o^- = (\rho_1 + \gamma_0 \alpha) \tilde{V}_o^+}$$

* Knowing \tilde{V}_1^+ in terms of \tilde{V}_o^+ we can rewrite as:

$$\tilde{V}_1^+ = \gamma_1 \tilde{V}_o^+$$

$$\tilde{V}_1^- = S_2 e^{-j2B_1 \Delta} \tilde{V}_1^+ * \alpha = S_2 e^{-j2B_1 \Delta}$$

$$\boxed{\tilde{V}_1^- = \alpha \tau_1 \tilde{V}_0^+} * \tilde{V}_1^+ = \tau_1 \tilde{V}_0^+$$

And:

$$\tilde{V}_2^+ = \tau_2 \tilde{V}_1^+ e^{-j(B_2 - B_1) \Delta}$$

$$\boxed{\tilde{V}_2^+ = \tau_2 \tau_1 e^{-j(B_2 - B_1) \Delta} \tilde{V}_0^+}$$

9.2.2

1) Show that $V(z,t) = V^+ [\cos(\omega t - Bz) + \rho \cos(\omega t + Bz)]$ ①

can be written as: $V(z,t) = A \cos(\omega t) \cos(Bz) + B \sin(\omega t) \sin(Bz)$ ②

First from eqn ① can be expanded using the following trig identity:

$$\cos(\alpha + \beta) = \cos(\alpha) \cos(\beta) - \sin(\alpha) \sin(\beta)$$

$$\cos(\alpha - \beta) = \cos(\alpha) \cos(\beta) + \sin(\alpha) \sin(\beta)$$

Then Eqn ① becomes:

$$V(z,t) = V^+ \left\{ [\cos(\omega t) \cos(Bz) + \sin(\omega t) \sin(Bz)] + \rho [\cos(\omega t) \cos(Bz) - \sin(\omega t) \sin(Bz)] \right\}$$

$$V(z,t) = V^+ \left\{ (1 + \rho) \cos(\omega t) \cos(Bz) + (1 - \rho) \sin(\omega t) \sin(Bz) \right\}$$

$$\therefore A = V^+ (1 + \rho)$$

$$B = V^+ (1 - \rho)$$

2) Code developed to animate V^- w/ amplitude $\frac{1}{2}$

3) From the animation we can see that V^+ & V^- will construct together or be destructive at times.

$$V_z = V^+ + V^-$$

$$|V_z|_{max} = 1 + 0.5 = 1.5$$

$$|V_z|_{min} = 1 - 0.5 = 0.5$$

Then the standing wave ratio will yield

$$S = \frac{1.5}{0.5} = 3$$

$$\therefore S = \frac{S-1}{S+1} = \frac{2}{4} = \frac{1}{2}$$

which corresponds to output of system w/ $V^- = 8V^+ = \frac{1}{2}V^+$

- 4) Similar things occur when boundary is shifted, position of boundary has no effect of results for Amplitudes
But because waves do not encounter in same spot,
a phase shift is then encountered.