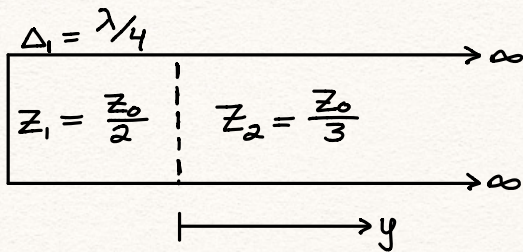


10.1 Impedance Transformation I

Given the Following Transmission line:



Compute $\tilde{\rho}_1(0)$ & $Z_1(-\lambda/4)$ by hand and using Smith Chart

10.1.1 Hand Calculation

Impedance Continuity states:

$$Z_1(0) = Z_2(0)$$

where Spatially dependence says:

$$Z_n(y) = Z_n \left(\frac{1 + \tilde{\rho}_n(y)}{1 - \tilde{\rho}_n(y)} \right)$$

$$Z_1 \left(\frac{1 + \tilde{\rho}_1(0)}{1 - \tilde{\rho}_1(0)} \right) = Z_2 \left(\frac{1 + \tilde{\rho}_2(0)}{1 - \tilde{\rho}_2(0)} \right)$$

Since Z_2 impedance line goes to infinity, then no reflected wave is produced

thus $\tilde{\rho}_2(y) = 0$ for all y

$$\therefore \frac{1 + \tilde{\rho}_1(0)}{1 - \tilde{\rho}_1(0)} = \frac{Z_2}{Z_1} \quad * \quad Z_1 = \frac{Z_0}{2}, \quad Z_2 = \frac{Z_0}{3}$$

$$\frac{1 + \tilde{\rho}_1}{1 - \tilde{\rho}_1} = \frac{2}{3} \quad * \quad \tilde{\rho}_n(y) = \tilde{\rho}_1 e^{2j\beta y} \rightarrow \tilde{\rho}_1(0) = \tilde{\rho} \quad (\text{some complex const})$$

$$1 + \tilde{\rho}_1 = \frac{2}{3} - \frac{2}{3}\tilde{\rho}_1$$

$$\frac{5}{3}\tilde{\rho}_1 = -\frac{1}{3}$$

$$\therefore \tilde{\rho}_1(0) = -\frac{1}{5}$$

$$\tilde{\rho}_1(y) = -\frac{1}{5} e^{j\frac{4\pi}{\lambda}y} \quad * \quad \beta = \frac{2\pi}{\lambda}$$

$$Z_1(-\lambda/4) = Z_1 \left(\frac{1 + \tilde{\rho}_1(-\lambda/4)}{1 - \tilde{\rho}_1(-\lambda/4)} \right) \quad * \quad \tilde{\rho}_1 = -\frac{1}{5} e^{-j\pi} = \frac{1}{5}$$

$$Z_1(-\lambda_1/4) = Z_1\left(\frac{1 + \cancel{1/5}}{1 - \cancel{1/5}}\right)$$

$$= Z_1\left(\frac{\cancel{6}^3}{\cancel{5} \cdot \cancel{4}_2}\right)$$

$$Z_1(-\lambda_1/4) = (3/2)Z_1$$

10.1.2 Smith Chart

1. Computing normalized impedance and associated normalized resistance r & x :

$$Z_1(0) = Z_2(0)$$

$$Z_1\left(\frac{1 + \tilde{\beta}_1(0)}{1 - \tilde{\beta}_1(0)}\right) = Z_2\left(\frac{1 + \tilde{\beta}_2(0)}{1 - \tilde{\beta}_2(0)}\right) \quad * \tilde{\beta}_2(0) = 0$$

$$\left(\frac{1 + \tilde{\beta}_1(0)}{1 - \tilde{\beta}_1(0)}\right) = \frac{Z_2}{Z_1}$$

$$\therefore \tilde{\beta}_1(0) = \left(\frac{Z_2/Z_1 - 1}{Z_2/Z_1 + 1}\right)$$

Normalized impedance is found as:

$$\frac{Z_2}{Z_1} = Z_3 = r + jx$$

$$\therefore r = Z_3, x = 0$$

2. from Smith Chart:

$$\tilde{\beta}_1(0) = -1/5$$

3. where:

$$\tilde{\beta}_1(-\lambda_1/4) = \tilde{\beta}_1(0) e^{j2\beta_1(-\Delta_1)} = \tilde{\beta}_1(0) * 2\beta_1(-\Delta_1) \quad * \phi = -2\beta_1\Delta_1 = -\pi$$

$$= 1/5 \text{ from Smith Chart using CW rotation of } -\pi \text{ from } \tilde{\beta}_1(0)$$

4. from the Smith Chart this yields:

$$r = 3/2, x = 0$$

5. Z_1 can be determined at $y = -\Delta_1$ as:

$$Z_1(-\Delta_1) = Z_1\left(\frac{1 + \tilde{\beta}_1(-\Delta_1)}{1 - \tilde{\beta}_1(-\Delta_1)}\right) \quad * \tilde{\beta}_1(-\Delta_1) = 1/5$$

$$= Z_1\left(\frac{1 + 1/5}{1 - 1/5}\right)$$

$$Z_1(-\Delta_1) = \frac{3}{2} Z_1$$

The Complete Smith Chart

Black Magic Design

