
10.1 Impedence Transformation II

Given the Following Transmission Line:

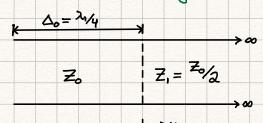

Compute:

2. Zo(-D1)

10.2.1 Hand Calculation

1. Impedance Continuity States:

$$Z_{o}(o) = Z_{i}(o)$$

Since Z, line exists and continues to oo, then no reflected wave exists:

$$Z_{\circ}\left(\frac{1+\widetilde{S}_{\circ}(o)}{1-\widehat{S}_{\circ}(o)}\right)=Z, \quad \#Z_{\circ}=\frac{Z_{\circ}}{2}$$

then § (0) can be found as:

$$\widetilde{\mathcal{G}}_{o}(0) = \left(\frac{\mathbb{Z}_{1/2_{o}-1}}{\mathbb{Z}_{1/2_{o}+1}}\right)$$

$$= \left(\frac{\frac{1}{2}-1}{\frac{1}{2}+1}\right)$$

:.
$$\widetilde{\mathcal{G}}_{0}(0) = -\frac{1}{3}$$

2. To find Zol-A,), phase is added to Soly:

$$\widetilde{S}_{0}(-\Delta_{0}) = -\frac{1}{3}e^{j2R(-\Delta_{0})}$$
 $*B = \frac{2\pi}{\lambda_{0}}$
 $\& \Delta_{1} = \frac{\lambda_{1}}{\lambda_{2}}$

$$\widetilde{S}_{0}(-\Delta_{0}) = -\frac{1}{3}e^{-j\pi} \lambda_{1}\lambda_{2}$$
 * if $\lambda_{1} = \lambda_{0}$

$$Z_o(-\Delta_o) = Z_o\left(\frac{1+\widehat{S}_o(-\Delta_o)}{1-\widehat{S}_o(-\Delta_o)}\right)$$

$$=Z_{o}\left(\frac{4/3}{2/3}\right)=2Z_{o}$$

1. Normalized impedance says:

$$\frac{Z_{i}(o)}{Z_{o}(o)} = \frac{1}{2}$$

then
$$r = 4$$
, $x = 0$

2. From Smith Chart

3. Finding So (- 20/4):

$$\widehat{S}_{o}(-\frac{1}{2}) = \widehat{S}_{o}(o)e^{-j\frac{4\pi}{2o}\frac{\lambda_{o}}{4}}$$

$$= \widehat{S}_{o}(o)e^{-j\pi}$$

$$\widetilde{\mathcal{G}}_{6}(-\frac{\lambda_{2}}{4}) = -\widetilde{\mathcal{G}}_{6}(0) = \frac{1}{3}$$

4. From a CW rotation of TI, the Smith Chart reads:

5. Then

$$Z_{o}(-\frac{2}{4}) = Z_{o}\left(\frac{1+\frac{6}{3}(-\frac{2}{4})}{1-\frac{6}{3}(-\frac{2}{4})}\right)$$
$$= Z_{o}\left(\frac{1+\frac{1}{3}}{1-\frac{1}{3}}\right)$$
$$= Z_{o}\left(\frac{\frac{1}{3}}{3}\cdot\frac{3}{2}\right)$$

The Complete Smith Chart

Black Magic Design

