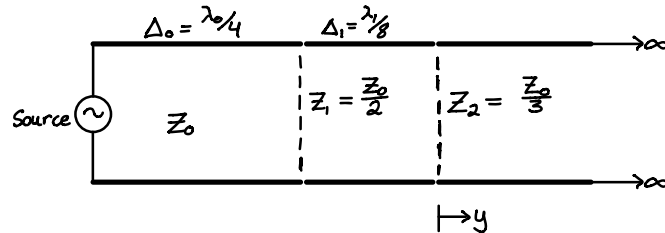


10.3 Impedance Transformation II

Given the following Transmission line:



10.1.3 Hand Calculation

Impedance Continuity states:

$$Z_1(0) = Z_2(0)$$

Since Z_2 line continues to ∞ , $\tilde{\Gamma}_2(y) = 0$ due to no reflected wave, then:

$$Z_1 \left(\frac{1 + \tilde{\Gamma}_1(0)}{1 - \tilde{\Gamma}_1(0)} \right) = Z_2$$

then $\tilde{\Gamma}_1(0)$ can be found as:

$$\tilde{\Gamma}_1(0) = \left(\frac{Z_2/Z_1 - 1}{Z_2/Z_1 + 1} \right) \quad * \quad \frac{Z_2}{Z_1} = \frac{Z_0/3}{Z_0/2} = \frac{2}{3}$$

$$\tilde{\Gamma}_1(0) = \left(\frac{2/3 - 1}{2/3 + 1} \right) = -1/5$$

Then:

$$\begin{aligned} \tilde{\Gamma}_1(-\lambda/8) &= \tilde{\Gamma}_1(0) e^{j 2 \frac{2\pi}{\lambda} \frac{\lambda}{8}} \\ &= \tilde{\Gamma}_1(0) e^{j \pi/4} \\ &= -j 1/5 \end{aligned}$$

From this the impedance $Z_1(-\lambda/8)$ can be found:

$$\begin{aligned} Z_1(-\lambda/8) &= Z_1 \left(\frac{1 + \tilde{\Gamma}_1(-\lambda/8)}{1 - \tilde{\Gamma}_1(-\lambda/8)} \right) \\ &= Z_1 \left(\frac{1 - j 1/5}{1 + j 1/5} \right) \left(\frac{1 - j 1/5}{1 - j 1/5} \right) \\ &= Z_1 \left(\frac{(1 - j 1/5)^2}{1 + 1/25} \right) \\ &= Z_1 \left[\left(\frac{1 - j 1/5}{1 + 1/25} \right) - j \left(\frac{2/5}{1 + 1/25} \right) \right] \end{aligned}$$

$$Z_1(-\lambda_g) = Z_1\left(\frac{l}{2} - j \frac{g}{2}\right) = Z_1(1e^{-j0.1257\pi}) \quad * \tan^{-1}\left(\frac{g}{l}\right) \approx 0.1257\pi$$

then from 2nd Boundary at $-\lambda_g$:

$$Z_o(-\lambda_g) = Z_1(-\lambda_g)$$

$$Z_o\left(\frac{1+\tilde{S}_o(-\lambda_g)}{1-\tilde{S}_o(-\lambda_g)}\right) = Z_1 e^{-j0.1257\pi}$$

$$\frac{1+\tilde{S}_o(-\lambda_g)}{1-\tilde{S}_o(-\lambda_g)} = \frac{Z_1}{Z_o} e^{-j0.1257\pi}$$

$$S_o(-\lambda_g) = \left(\frac{\frac{Z_1}{Z_o} e^{-j0.1257\pi} - 1}{\frac{Z_1}{Z_o} e^{-j0.1257\pi} + 1} \right) * Z_1 = Z_o/2$$

$$\tilde{S}_o(-\lambda_g) = \left(\frac{\frac{1}{2} e^{-j0.1257\pi} - 1}{\frac{1}{2} e^{-j0.1257\pi} + 1} \right)$$

Computing w/ MATLAB

$$\therefore \tilde{S}_o(-\lambda_g) \approx 0.388 \angle -152.85^\circ = -0.8492\pi$$

then:

$$S_o(-\Delta_1, -\Delta_o) \approx 0.388 e^{-j0.8492\pi} e^{j\frac{4\pi}{20} \frac{2l}{\lambda}} \quad * \text{if } \lambda_o = \lambda_l$$

$$\begin{aligned} \tilde{S}_o(-\Delta_1, -\Delta_o) &= 0.388 e^{-j0.8492\pi} e^{j\pi} \\ &= 0.388 e^{j0.1508\pi} \end{aligned}$$

impedence at source can be found as:

$$\begin{aligned} Z_o(-\Delta_1, -\Delta_o) &= Z_o \left(\frac{1+\tilde{S}_o(-\Delta_1, -\Delta_o)}{1-\tilde{S}_o(-\Delta_1, -\Delta_o)} \right) \\ &= Z_o \left(\frac{1-0.388 e^{j0.1508\pi}}{1+0.388 e^{j0.1508\pi}} \right) \end{aligned}$$

$$Z(-[\Delta_1, \Delta_o]) = Z_o (2 e^{j0.8492\pi})$$

$$= 2Z_o \angle -152.85^\circ$$